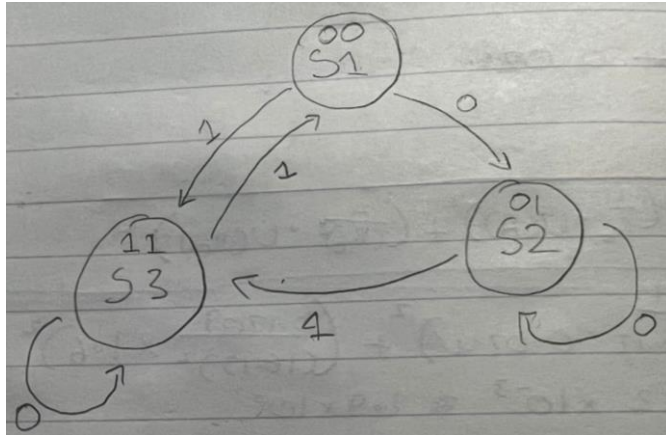


### Exercise 3

#### State Diagram:

First, we make a state diagram to get better understanding of our states to make transition state table later on.



#### State Table:

We will be using the D-Flip Flops to hold the bits for our states, D-flipflops have only one input and their input depends on the previous one.

	Present State	Input	Next State	D1	D2	Output
S1	00	0	01	0	1	0
		1	11	1	1	0
S2	01	0	01	0	1	1
		1	11	1	1	0
S3	11	0	11	1	1	0
		1	00	0	0	1

#### Karnaugh Map:

Now we make the Karnaugh Map for D1 and D2 to find the functions to make our circuit.

BX					
A		00	01	11	10
	0	0	0	1	0
	1	1	1	0	0


$$D1 = B\bar{A} + BX\bar{A}$$

		BX			
A		00	01	11	10
	0	1	1	1	0
	1	1	1	0	0

$$D2 = \sim A + B$$

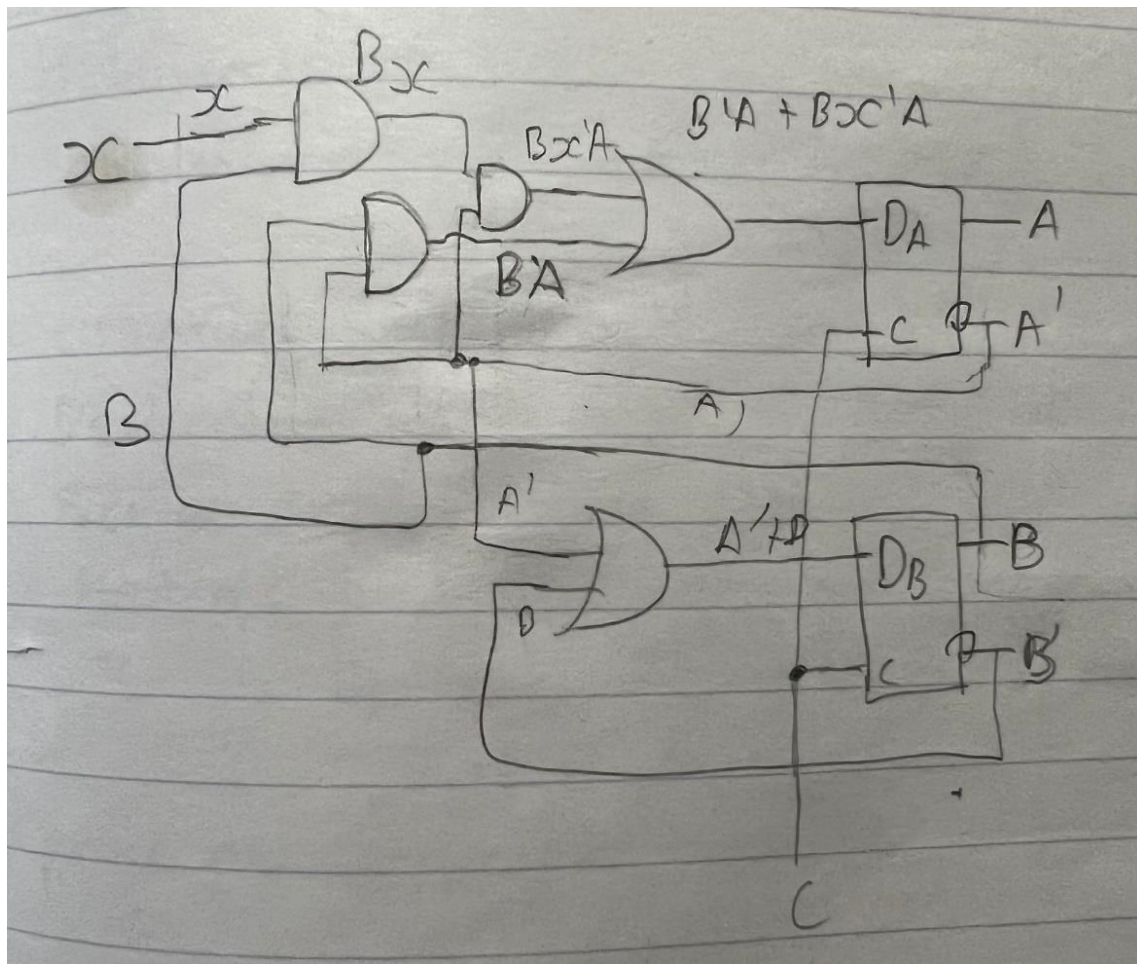
### Circuit (OR, AND, NOT):

Here we create the circuit using AND and OR gates and 2 D-Flipflops




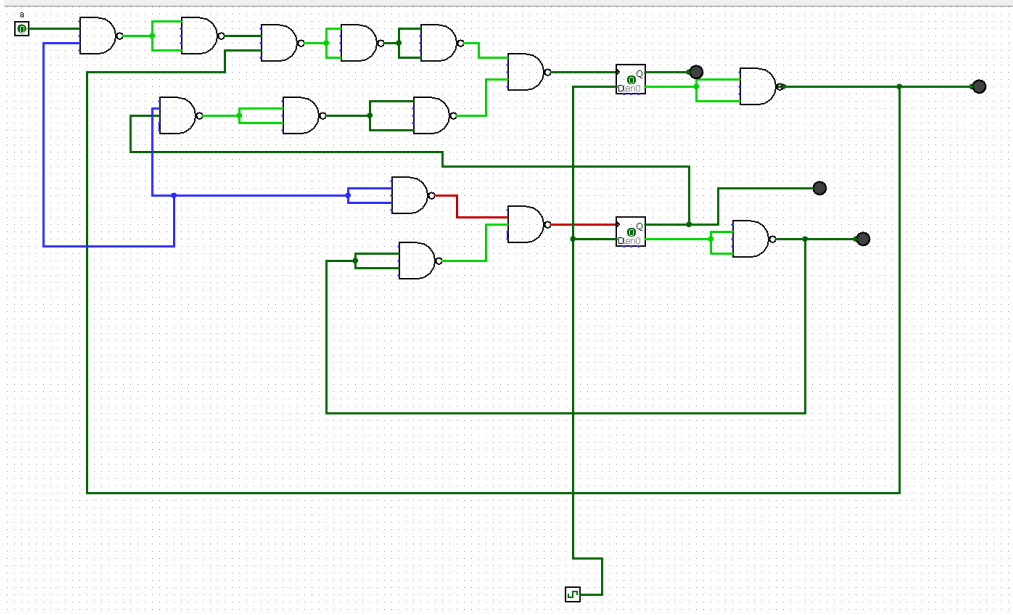**Conversion of Circuit(NAND ONLY):**

Now we use the conversion rules for AND,OR gate to NAND gates to make the final NAND gate circuit only.



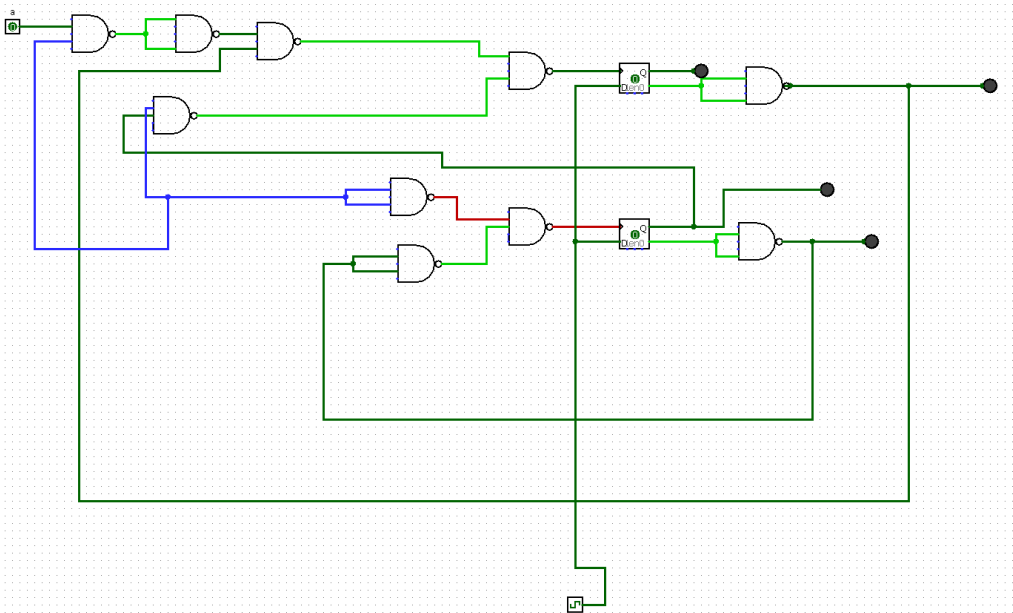Now we cancel the invertors that are in the same rule because  $\sim a \sim a = a$



**Conclusion:**

We started off with creating a diagram to get a better understanding of the states, we then used that diagram to make the state transition table to get our values for D1 and D2 so we can make the excitation table for D1 and D2 to get the functions( $D1 = B\bar{A} + BX\bar{A}$  ,  $D2 = \bar{A} + B$ ) that we require to create a sequential circuit using 2 D-flip flops and AND,OR gates then we convert the gates to invertors and Nand gates and cancel the ones in the same row to get our final NAND sequential circuit.